



Faculty of Engineering and Technology
Electrical and Computer Engineering Department
second semester 2020/2021
CIRCUIT ANALYSIS ENEE2304
CIRCUIT ANALYSIS PROJECT

Prepared by: Musab Masalmah 1200078

Instructor: Dr. Hakam Shehadeh

Section: SECTION_2

Date: 2022/6/10

Table of Contents


Introduction	3
First Quastion	4
The drawing	4
Secouned Quastion	5
The drawing.....	6
Sec A	6
Sec B	7
Sec C	7
Sec D	8

Introduction:

At first, I had to solve this project, so I went to the Internet and YouTube to learn how the program works, and then I started solving the first question, which is about:


-First question:

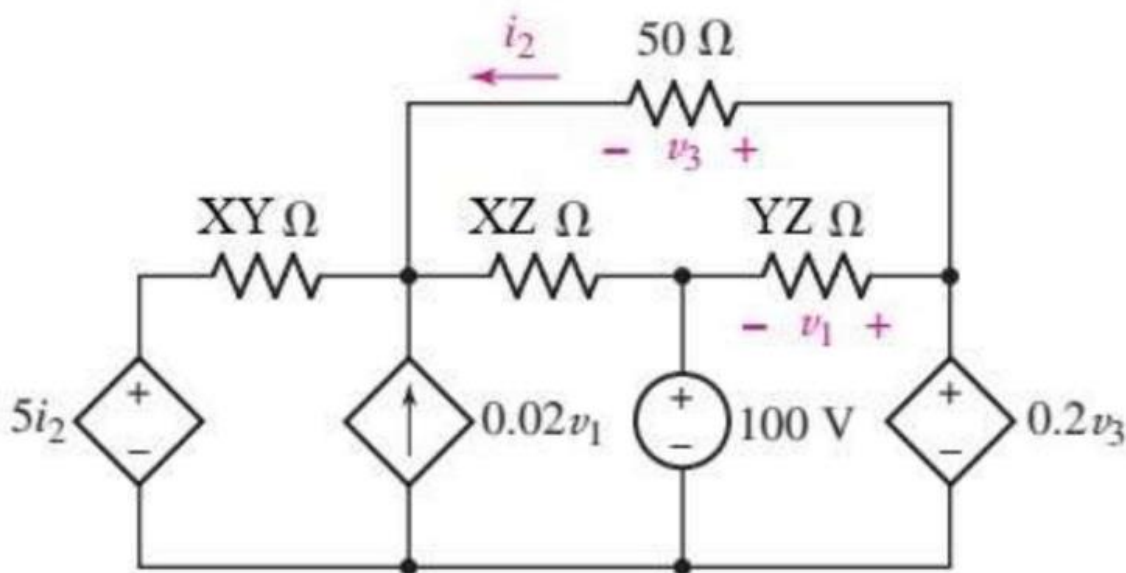Question 1: Construct a PSPICE schematic for the circuit shown in the figure below. Simulate the schematic and show voltages at each node and current in each branch.



The drawing

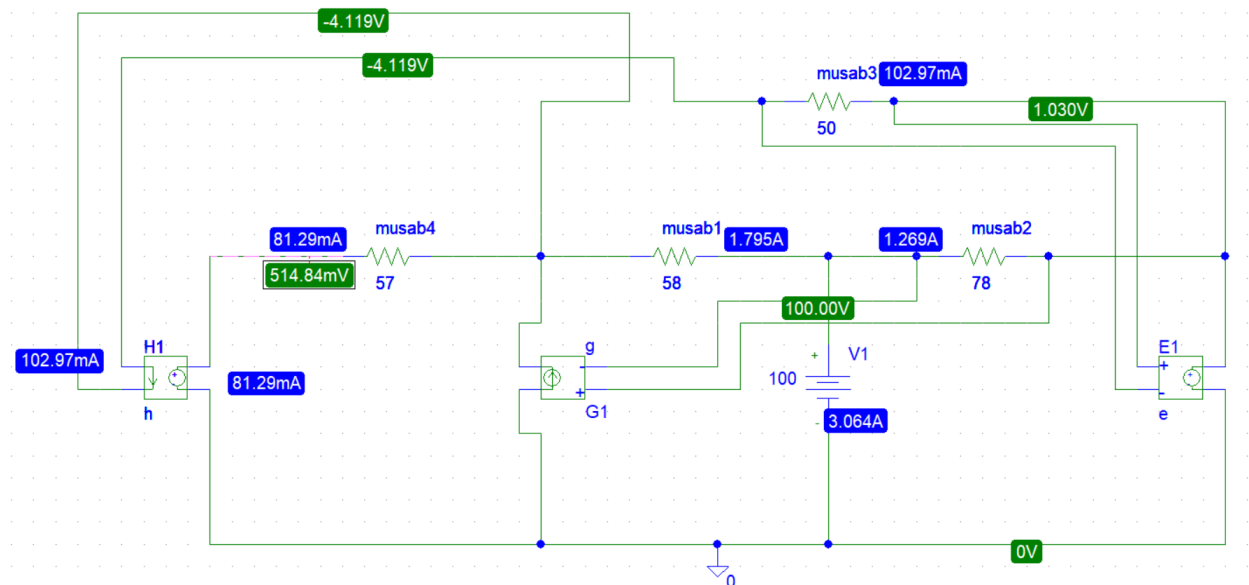Then I drew the circuit on the program and show voltages at each node and current in each branch and it looked like this:



-With this, I have finished most of the first question.

-Secoured question:

I read the text of the second question and it states the following:


Question 2: The circuit shown in Figure below has two inputs, $v_s(t)$ and $i_s(t)$, and one output, $v(t)$. When inputs are given by $V_s(t) = V_m \sin 6t$ V and $i_s(t) = I_m$ A the output will be $v_o(t) = A \sin(6t + \theta) + B$ V. Linearity requires that A be proportional to V_m and that B be proportional to I_m . Consequently, we can write $A = k_1 V_m$ and $B = k_2 I_m$, where k_1 and k_2 are constants yet to be determined.

(a) Use PSpice to determine the value of k_1 by simulating the circuit, using $V_m = 1$ V and $I_m = 0$.


(b) Use PSpice to determine the value of k_2 by simulating the circuit, using $V_m = 0$ V and $I_m = 1$.

(c) Knowing k_1 and k_2 , specify the values of V_m and I_m that are required to cause $v_o(t) = 5 \sin(6t + \theta) + 5$ V. Simulate the circuit, using PSpice to verify the specified values of V_m and I_m .

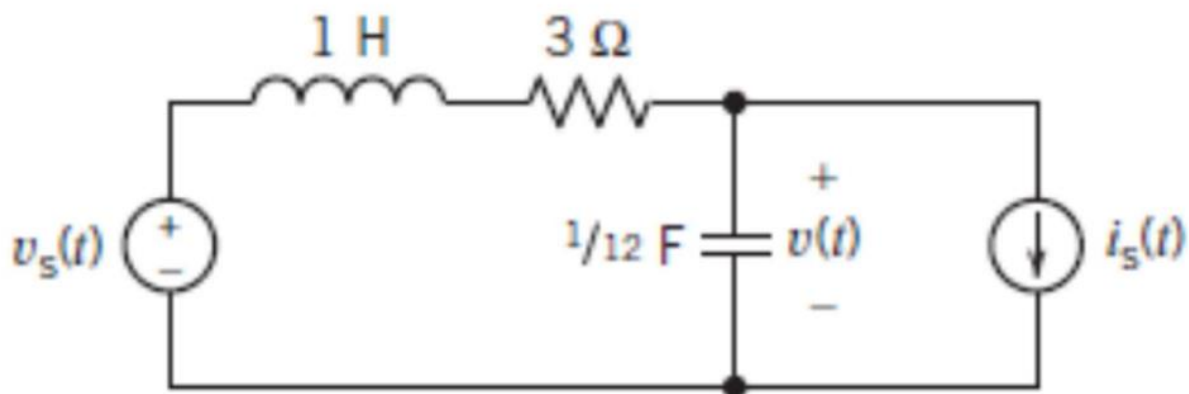
(d) Determine the average power delivered by $v_s(t)$ using Pspice.



-The Drawing:

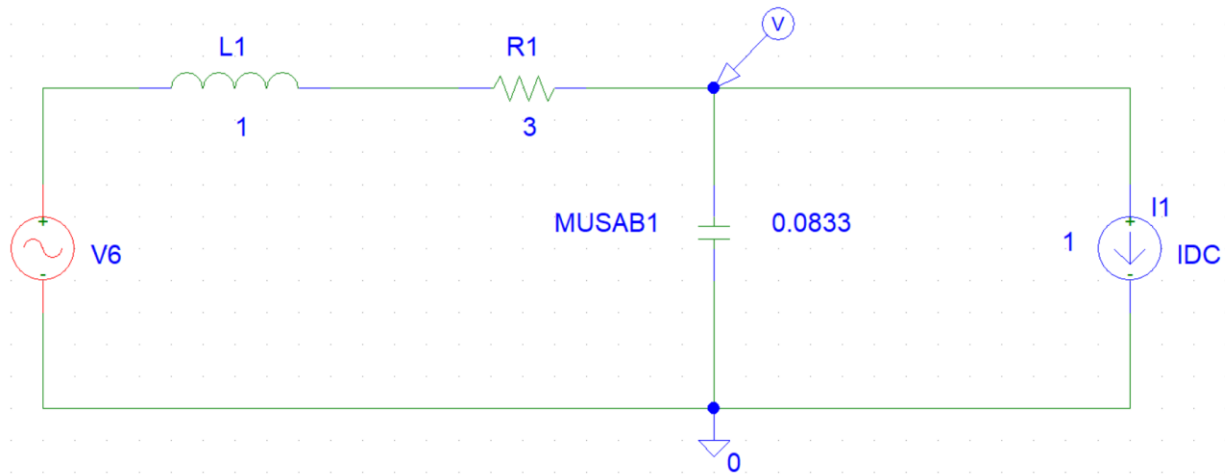


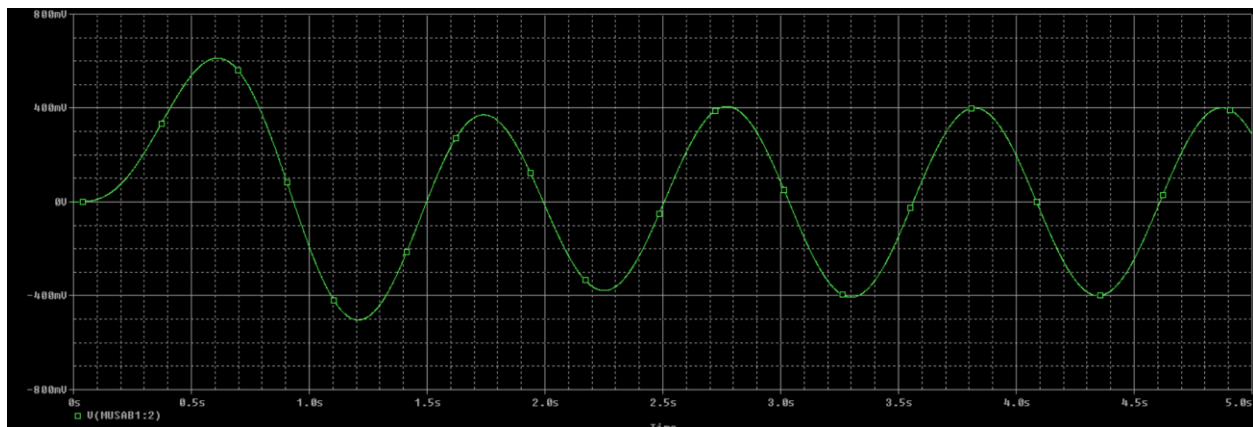A) The same in the first branch, which was required to put the value of the current to zero and the value of the source one



$$K1 = A / V_m \quad \rightarrow \quad K1 = 0.405/1 \quad \rightarrow \quad K1 = 0.405$$

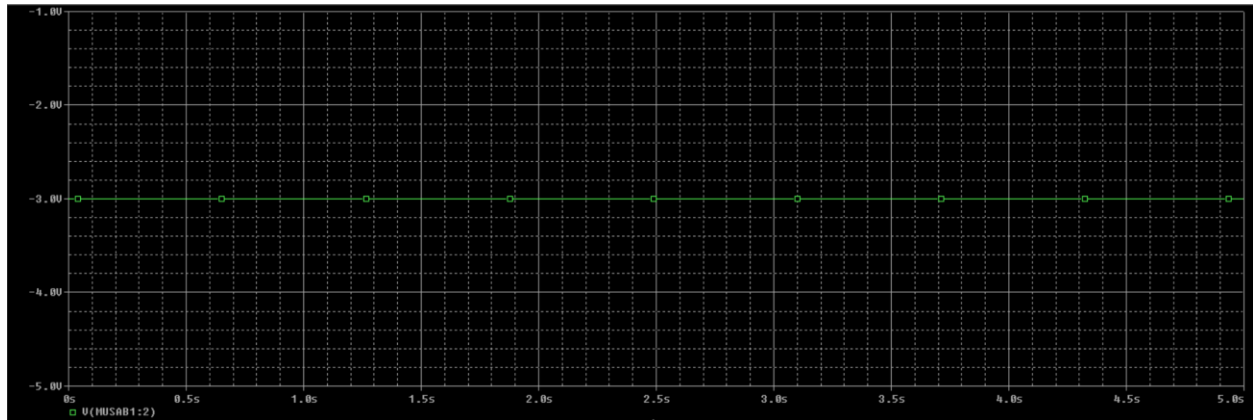B) The same in the first branch, which was required to put the value of the current to one and the value of the source zero




$$K2 = B / I_m \quad \rightarrow \quad K2 = -3/1 \quad \rightarrow \quad K2 = -3$$

C) Put the values of V_m and I_m :

$$V_m = A / k_1 = 5 / 0.405 = 12.35$$

$$I_m = B / k_2 = 5 / -3 = -1.67$$

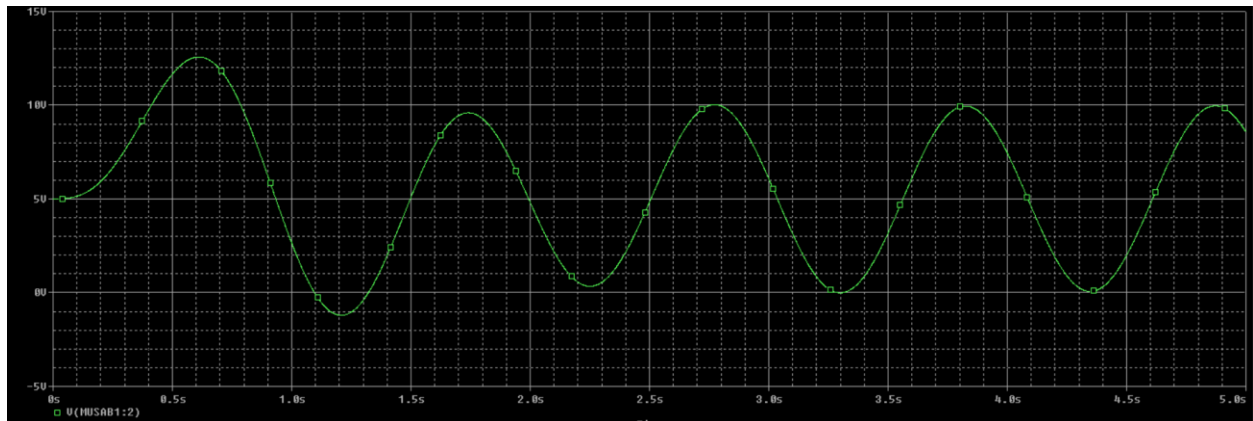

D) Find the average power delivered by $v_s(t)$ by the simulation and get the draw of the power by $AVG(V1(V6) * I(V6))$

